

CS 7260 - Internet Architecture & Protocols

Scribe – 8/27

As discussed in the last class, In the case of priority encoder -

If Input = 0, the output is 0

If Input = 1, the output is 1

- **Programmable Priority Encoder**

In Programmable Priority Encoder (PPE) there is an additional input where user can specify a number K which becomes the starting point of our scan. There is an N -bit input I as before, together with an additional $\log N$ -bit input P . The PPE circuit must compute an output O such that $O[j] = 1$, where j is the first position beyond P (treated as a binary value) that has a nonzero bit in I .

 


Fig 1: A Sample PPE. Here If $I_k = 1$, then $O_k = 1$

- A simple solution for PPE can be implemented as following

“A barrel shifter can be used at the starting input bits to shift the bits to the left by $(K-1)$ positions, after that we can feed the output of this barrel shifter to a simple Priority encoder. Then to get the desired output, we use another barrel shifter to shift the bits to the right by $(K-1)$ positions.”

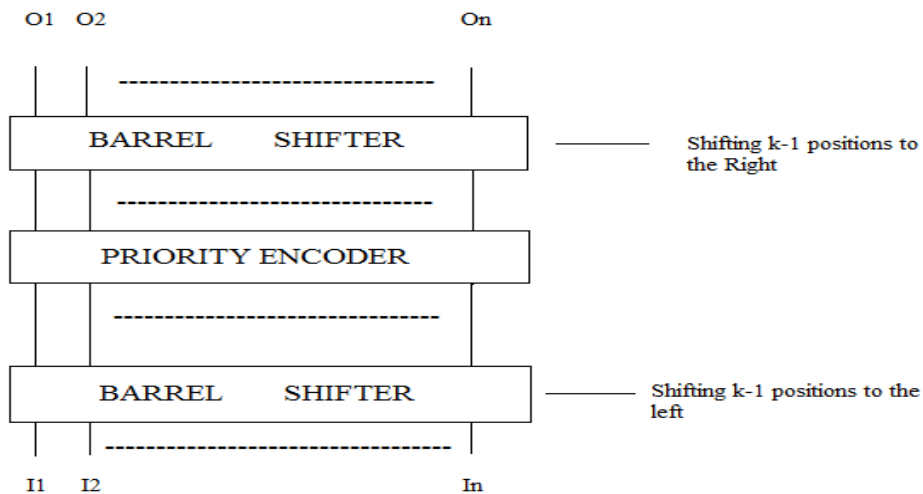


Fig 2: A Naïve Simple Solution for PPE

Now the question arises as to whether there should be a digital circuitry to subtract 1 from K ? The answer would be a NO as this depends on the convention decided for the input Value (I). For e.g. , If we would have taken the first Input to be I_0 instead of I_1 , then there would have been no need of subtracting 1 from K .

Calculating the Delay: In the approach suggested above, a barrel shifter for N bits Input can be implemented using a tree of 2-input multiplexers in around $\log N$ time. Thus for the 2 barrel shifters and 1 Priority Encoder, the total gate delay becomes greater than equal to $3 \log N$.

- Another way in which we can describe the PPE is that :

“If the input has some bit set at position K or higher than priority encode among bit positions k or higher else priority encode among the original Input”

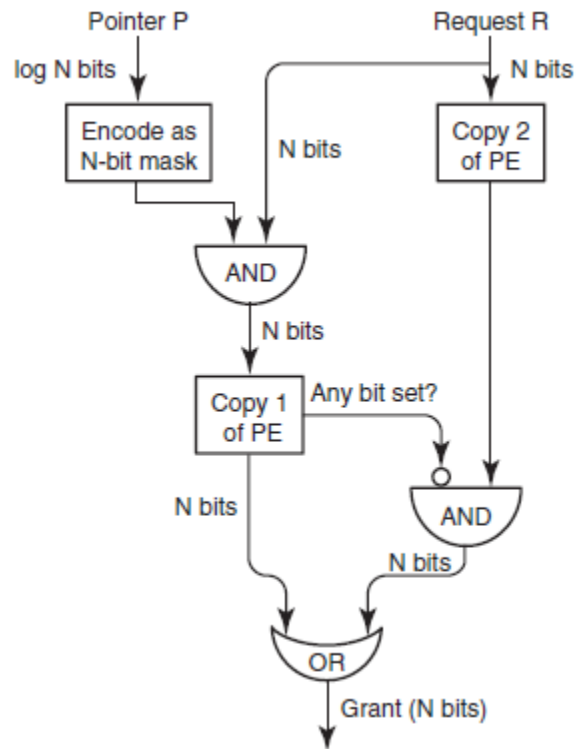


Fig 3: The design uses copy 1 of a priority encoder to find the highest bit set, if any, of all bits greater than P using a mask encoding of P. If such a bit is not found, the output of a second copy of a priority encoder is enabled using the bottom AND gate. The results of the two copies are then combined using an N-input OR gate.

Calculating the Delay: Here as we have split the problem into 2 ways, One where some bit is set after position P and the second where no bit is set. We are calculating the output accordingly as per the situation, so the overall delay gets reduced. Here, the gate delay will become $2\log N$.

- **Memories**

Here we look at the different memory technologies which are available to us and the corresponding memory access time for each.

Registers- A register is an ordered collection of flip-flops

Access Delay : 0 – 5 nsec.

SRAM- Stands for Static Random Access Memory. Contains N registers addressed by log N address bits.

Access Delay : 1-2 nsec (for on chip SRAM)
5-10 nsec (for off chip SRAM)

DRAM- Stands for Dynamic Random Access Memory. Here, suppose we have to access a page of 512 bytes. In the case of DRAM to access the first byte, it will take around 40 or 50 nsec. After that for every other byte, it takes 1-2 nsec.

Access Delay : 40-60 nsec

-----X-----

References: Other than the lecture, I have referred the text book - Network Algorithmics by *George Varghese*